

ENGS 31 Final Project Report: The Calculator

Gavin Burns and Sarah Hutchinson

August 2021

Abstract

The goal of our project was to use digital electronic design to create a calculator that can add, subtract, multiply, and divide numbers with results up to 3 digits. Our resulting design uses a computer-connected universal asynchronous receiver-transmitter system (UART) to send signals to the FPGA, where the calculations take place. The calculation process and results are outputted to the 7-segment display on the FPGA, with additional features such as LEDs to indicate which step of the entry process is occurring, and buttons to view past operand entries.

Contents

1	Introduction	3
2	Design Solution	3
2.1	Specifications	3
2.2	Operating Instructions	3
2.2.1	Setup	3
2.2.2	Communicating	4
2.2.3	Display	4
2.3	Theory of Operation	4
2.3.1	Top Level Design	5
2.3.2	UART	5
2.3.3	ASCII Converter	5
2.3.4	Main Controller	6
2.3.5	Main Datapath	6
2.3.6	Math Block	6
2.3.7	Binary to BCD	7
2.3.8	Display	7
3	Evaluation	7
3.1	Functionality	7
3.2	Review	8
4	Conclusions	8
5	Acknowledgements	8
6	References	8

1 Introduction

For our final project in ENGS31 we were tasked with designing a hardware calculator in VHDL. Specifically, we wanted a calculator that could represent integers between -999 to 999, carry the four main mathematical operations(+ - * /), and be able to recursively apply answers to the next equation. Using processes and ideas we've learned throughout the term we came up with a thorough design and began working. Over the course of the project we practiced top-down circuit design and many different debugging techniques. Furthermore, we added some ease of life capabilities and additive features to separate our design from a simple calculator.

2 Design Solution

2.1 Specifications

Our calculator takes inputs coming from a connected computer, manipulates entered values and operators within the FPGA (calculator functions), and outputs values and results onto the FPGA seven-segment display. Values come into the system through a universal asynchronous receiver-transmitter (UART) system. This is a form of serial input. Using the Waveforms application on the computer, we enter numbers and operators which are then sent to the FPGA, coded as an ASCII code in serial. Our calculator connected to the computer via Analog Discovery 2 (transmits signal). Data is sent from the computer at a baud rate of 115.2k. This rate refers to how many different signals occur per second. This is relevant because since the UART is asynchronous, a clock signal is not sent to the FPGA and therefore it is necessary to use the baud rate to determine how to read the incoming signal. Our system is clocked at 1MHz, which means that a new signal is sent from the computer approximately every 8 clock cycles. Our calculator outputs to the 7-segment display on the FPGA, as well as to the LED lights. Depending on what part of the calculation process is occurring, either the operands, a decimal point to indicate which operator is in use, or the answer is displayed on the board. One of four LED lights illuminates at any given time to indicate which part of the calculation is occurring and what the next entry should be from the user (waiting for operand, waiting for operator, showing answer, or overflow). Additionally, there are input buttons on the FPGA which can be pressed to view past operands on the 7-segment display.

2.2 Operating Instructions

2.2.1 Setup

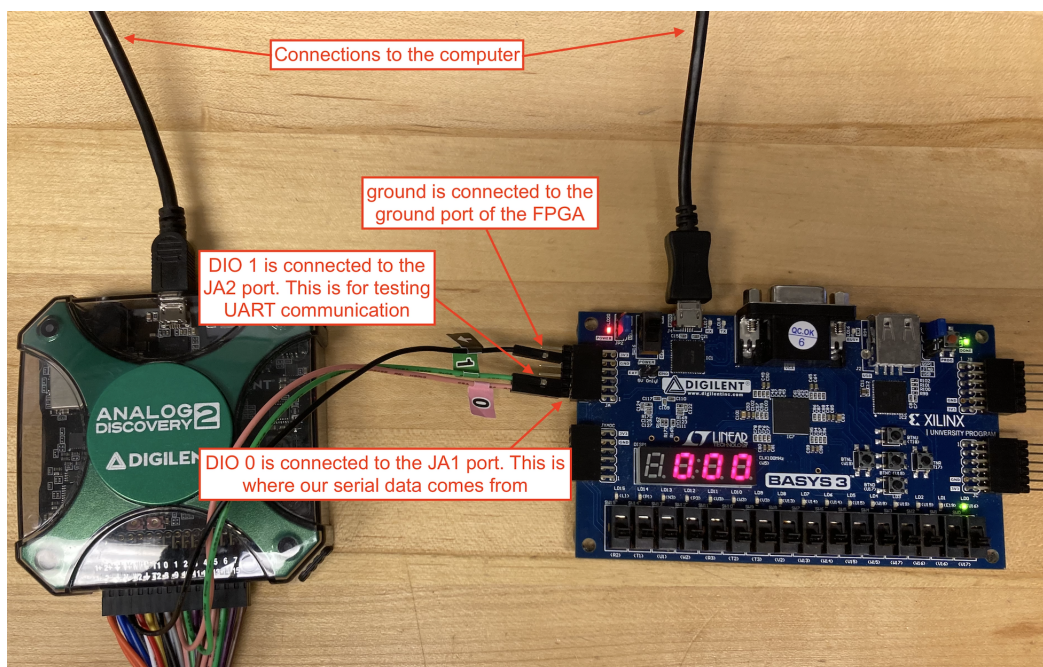


Figure 1: AD2 and FPGA connections. DIO 0(pink) and 1(green) are used to send and receive signals from the AD2 to FPGA respectively. Additional connections are made individually between the Ad2 and FPGA to the computer. Signals are typed in via a keyboard, sent through the AD2 and finally delivered to the FPGA via serial data.

In order to operate our calculator it is important to understand how to set it up. Since we are using a FPGA and AD2 converter we'll need to connect the data ports together to communicate between them. According to our constraints file in the Appendix, we will be using the DIO 0 and DIO 1 wires on the AD2 to control the transmission and receiving of signals respectively. On our FPGA, the JA1 port is where our serial data from the computer comes from, so we'll connect the DIO 0(pink cable) wire to the JA1 port. Likewise, the JA2 port is the transmission port of our FPGA back to the AD2 and computer monitor. Although we used this port for checking UART capabilities and debugging you can connect this port to the DIO 1 wire as shown in the figure above. Do not forget to also connect the ground wire of the AD2 to any ground port on the FPGA. For ease of use we used the ground port closest to the AD2 (JA5).

Lastly, the micro USB ports for both the FPGA and AD2 are connected to the computer to provide power and allow us to enter digits into the calculator via the keyboard.

2.2.2 Communicating

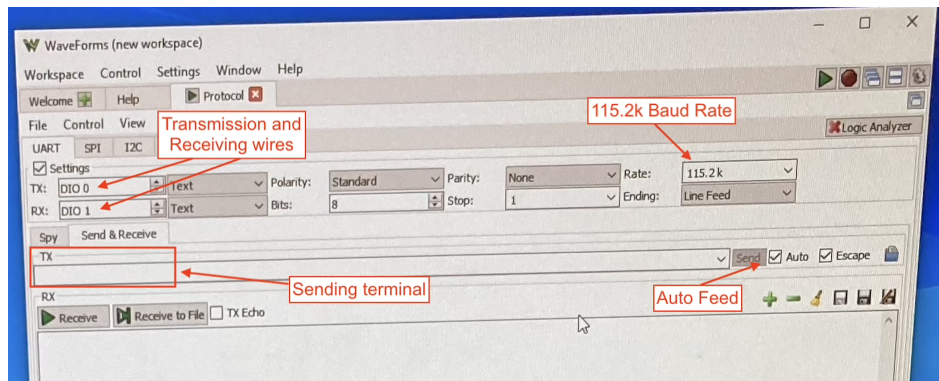


Figure 2: UART Protocol workspace for the Waveforms application. In it you can send data in the sending terminal, set your baud rate, identify transmission and receiving wires, as well as view any receiving signals in the Rx window.

In order to communicate with the calculator, we'll be using the Waveforms app provided by the AD2 to send serial signals to the FPGA. In the protocol workspace, we can send serial data to our system to be processed and displayed on the seven segments displays.

As shown in the figure above it is important to set the baud rate to 115.2k to make sure serial communication is synchronized between the computer and the FPGA.

In the transmission terminal window you can type in inputs to be sent to the AD2 and subsequently the FPGA. In our tests it was helpful to set the feed to auto send such that we wouldn't need to press enter after each input to successfully send it.

2.2.3 Display

 


Figure 3: FPGA Display for Calculator. The four seven segment displays show the negative and 3 digits of the inputted and calculated numbers. Decimal points are used to indicate operators(+ - * /). LEDs in the bottom right corner indicate current state of the equation. Starting with operand A and moving to operator, operand B, and Answer.

When entering data from the keyboard it is important to receive some form of feedback to clarify your entering the correct digits. When using our calculator digits will appear in the seven segment display on the FPGA. Our calculator is reserved to only storing 3 digits so the fourth segment will be used to display the negative sign of the number.

Additionally, valid operators will be displayed as specific decimal points found in the bottom right corner of each segment. Only one decimal point will be lit up at any given time and moving left to right on the FPGA, they represent the division, multiplication, subtraction, and addition.

The LEDs on the bottom right of the board are used to communicate to the user the current state of the equation. In the figure above, the rightmost LED is on, indicating that the user will be inputting the A operand. Moving leftward, the second LED represent entering an operator, the third LED is for the B operand, and the fourth LED is on when an answer is being displayed.

The last feature we have for the display is the control of the top and bottom buttons of the FPGA to display the currently stored A and B operands. When the top button is pressed, the current display will be overwritten to show the A operand used in the equation. The same goes for the B operand when you press the bottom button.

2.3 Theory of Operation

The following steps indicate the typical flow of use for a person using our calculator: (See Figure 11 in Appendix 1.)

Step 1: The user inputs an integer operand between -999 to 999 one digit at a time

- Step 2: The user inputs their desired operation between addition, subtraction, multiplication, and division
- Step 3: The user inputs their second integer operand between -999 to 999, which will enact their desired operation on the previous operand
- Step 4: The user receives an answer to their equation and can either chose to start a new equation(return to step 1) or save this answer and chain it into another equation(move to step 2)

2.3.1 Top Level Design

Before diving into the details of each component, we first figured out what problems we'd come across and describe how our deign plans to overcome them.

Starting to our problem with transmitting to the FPGA, we decided to use UART to process the serial data inputted from our computer and turn it into a single code.

As shown in Figure 5 in Appendix 1, this code would then be fed through an ASCII Converter to interpret the code as one of many keyboard inputs and output the necessary signals. Operators will receive a 2-bit code to differentiate the 4 potential operators; digits will receive there associated 4-bit BCD code; and the negative, enter, and delete keys will all get a single standard logic signal.

Signals sent from the ASCII Converter would then be read by the Controller; which in turn communicates with the Datapath; to organize and store most of this data. The Datapath works to shuttle in digits and operator in from the ASCII Converter and the Controller moderates when, where, and how many signals get stored.

Once all necessary data is collected, the controller will signal the Math Block to preform the calculation. Specifically, the Math Block converts the BCD numbers into signed binary which can then be used to calculate the answer.

Lastly, we decided to use a Binary to BCD converter to take our binary answer (and any other variables) and transform them into a BCD signal readable by the seven segment display. Likewise, other signals outputted by the Controller are given to the seven segment displays to select what should be displayed at each point in the calculation.

2.3.2 UART

The UART input component takes the serial input from the computer, which arrives at a rate of 115,200 signals per second, and compiles it into an 8-bit parallel signal which can be read by the ASCII converter to determine which value it represents (ASCII codes are 8 bits long). In order to understand how the UART reciever works, it is necessary to understand the components of a UART signal. A UART signal is 10 bits long. The signal is at 1 when it is idle, and the first bit is always 0. This is called the start bit and indicates that the next 8 bits will represent a value. The last bit is always 1, and is called the stop bit. The synchronizer uses two flip-flops to ensure that the incoming signal is being fed to the circuit at the 1MHz system clock speed. This is particularly important because the incoming UART signal is asynchronous. See Figure 6 in Appendix 1 for UART Block Diagram reference. The synchronized signal is passed into the deserializer shift register, which, in conjunction with the UART state machine, converts the serial signal to a parallel signal. The state machine starts in the idle state. See Figure 12 in Appendix 2 for UART State Diagram. When the first bit is detected to be a 0, the state machine moves into the count_baud_1 state. This sends a signal to the counter that to start counting. Since the signal comes in at a rate of 115,200 signals per second and the system is at 1MHz, in general, the counter in general counts to 8 before it enables timeout, which, causes the state machine to move to the shift_1 state, make shift_en high, and have the contents of the shift register to be shifted. It is ideal to read the incoming signal in the middle of the signal to get a steady value, so the count_baud_1 state enables timeout after 1 clock cycle, thus there is a different state for the subsequent counting and shifting states. After each shift, the shift counter increments. While the counter is counting, the shift counter holds its current value. Once there have been 10 shifts, the load state is entered, during which load_en is high and the contents of the shift registers are loaded into the parallel output.

See Figure 15 in Appendix 3 for the simulation image.

2.3.3 ASCII Converter

The goal of the ASCII converter is to take the 8-bit signal provided by the UART and decode it into specific signals. Knowing that the 8-bit signal (labeled as par_output in block diagram) represents a single key stroke from a keyboard, we deduced that it would be best to utilize a look-up-table to assign the input number to a specific output signal. (See Figure 7 in Appendix 1 for ASCII Converter Block Diagram).

To do this we first had to decide which keys would be registered to which signals. This was fairly straightforward and by using an ASCII look up table we were able to figure what the par_output code would be for keys associated with the numbers 0-9, all necessary operators(+ - * /), and the enter key. Consequently, both the backspace and delete key were not eligible inputs for the Waveform program that we were using to communicate with the system. Instead, we chose to register the spacebar as our primary delete key for the continuation of our project.

The actual hardware implementation of our ASCII Converter was just a look-up-table to check the input signal and set the corresponding output signals. For example; when the par_output signal is recognized to be some number, valid_int will go high and dig_code will parse the input into its BCD counterpart. The same goes for valid_op and op_code for when an operator code is detected, valid_neg for when the '-' key is detected, and entr/dlt for when the enter key or spacebar is detected.

For a more detailed analysis of the ASCII converter's operation please review ASCII Converter testbenches 1 (Figure 16) and 2 (Figure 17 in Appendix 3).

2.3.4 Main Controller

The crux of our calculator is the main controller that signals to many of the other components when to do each of their processes. (See 13 in Appendix 2 for Calculator State Diagram). Once data is decoded by the ASCII Converter it is up to the Controller to read these signals and move through its states, commanding the other components as it goes. The structure of the Controller's state machine is such that we can break down the flow of state into four individual sections (all of which are cycled through using the enter key).

The initial state of the machine begins in the first section that we'll call the "operands" section (colored in blue in the above figure). In this section, user inputs are read to store and delete numbers to form the A and B operands of the equation. Valid integers have the controller signal the datapath to store this number while the spacebar has the controller signal to delete the least significant digit currently stored. Furthermore, the minus symbol in this section is used to toggle the negativity of a number and other operator symbols have no effect on the system. Another feature that is present while in this section is a counter that is used to make sure the user does not input more than 3 digits. Our calculator has a capacity to work with numbers between -999 to 999, so it was important to us to keep the user within these bounds during number inputs. Upon leaving this section the controller will signal to take whatever 3-digit number that has been created and store it as the A or B operand as determined by the FLAG signal.

The FLAG signal is used to differentiate A operand from B operand storage. Upon storing a number in operand A, the signal toggles high to signal that the next number stored will be operand B. It is then toggled down when calculation is complete and the Restart state is reached.

The next section of states is the "operator" section (yellow). Similar to the operands section except user inputs are read to store and delete operators. In this section numbers have no effect and the minus key is registered as a minus symbol. Following this section, the Controller briefly enters the Clear state to make sure all previous digits have been cleared before returning to the Operand section.

After operand A, B, and an operator have been stored the next section the Controller goes to is "computation". This section signals the Math Block to compute an answer and waits to see if the user wishes to chain the answer with another equation or start again from scratch. If the answer generated, overflows the calculator's capacity then the Controller will move to the Overload state which requires the user to begin a new equation. Alternatively, any other numerical answer can be chained into a new equation by entering an operator. This will move the Controller into a brief buffer state to store the answer as the A operand before going to the final section.

The "chain operator" state (Red) is nearly identical to the "operator" section except for the signal_output signal. This signal (along with LED_output) communicates with the seven segment display to tell them which numbers to show. In order to show the answer and new operator at the same time, we needed to create this additional section with a separate signal_output code.

For a waveform clarification on the controller's operation, please see the Calculator Controller Testbench (Figure 18) in the Appendix 3.

2.3.5 Main Datapath

According to the operating instructions of our system, the user will enter in a single digit at a time to ultimately form a 3-digit number between -999 and 999. In order to take single digits and assemble them into full numbers, we needed a way to preserve their order as multiple numbers are entered; this is done in the calculator's Datapath. (See Figure 8 in Appendix 1 for Datapath Block Diagram).

When the dig_en signal is sent from the Controller, each number register receives the previous register's digit and num0 receives the newest dig_code from the ASCII converter. Likewise, when dig_dlt is sent, each number register is enabled to take in a new digit, but the digit they receive is taken from the register ahead of them.

As you can see in the diagram above the multiplexer determines where the data being stored comes from. Its select bit is the dig_dlt signal from the Controller; when low it sends the previous register's digit, and when high it sends the following register. It should also be noted that the num2 register will always be reset when the dig_dlt or dig_clr signals are passed to ensure that a zero is passed back to the previous register when the delete signal is sent.

This Datapath also controls the current state of the numbers' negativity. Whenever the neg_en signal is passed to the Datapath, the neg output will toggle between high and low with every press. We can also see in the figure above that the dig_clr signal also resets the current state of the neg register because negativity is very much tied to the actual number itself.

Lastly, the Datapath stores and outputs the current operator inputted into the system. When op_en is sent, the op_code from the ASCII converter is stored in the register and an op_full signal is sent back to the controller. This signal is to indicate that an operator has been stored and the user can officially move on to the next state.

A full waveform of the Datapath's operations can be viewed in Appendix 3 under Calculator Datapath Testbench. (Figure 19.)

2.3.6 Math Block

Following up on the calculator's Datapath, the Math Block takes in its digits (num0-2), negative, and operator to form an equation for computation. (See Figure 9 in Appendix 1 for Math Block Diagram).

As a reminder, the num signals from the Datapath represent the 3 digits of a base 10 number. So before computation num0, num1, num2 are turned into a single binary number by multiplying the hundreds digit (num2) by 100, the tens digit (num1) by 10, and adding them all together. Additionally, if a negative is present for this number then the system will perform a two's complement conversion to make the number a

negative. After this conversion, the new signed binary number is stored in operand A or B (as decided by the controller) until it is needed for computation.

Speaking of which, the computation performed is determined by the stored operator value also from the datapath. This can be seen as the multiplexer that takes its select bit as the op signal. This value is computed but not stored officially until the math_en signal is outputted high by the controller.

After an answer is calculated it is stored in the Answer_temp register and answer_full signal is fired directly back to the Controller. The new answer is then immediately checked to see if it exceeds the calculator's maximum value; if so the overflow signal goes high.

Likewise, after the an answer is generated, it runs through binary conditioning to separate the negative sign from the rest of the number. This is to make the outputting answer digestible for the binary to BCD converter while preserving the negativity of the number. The specific process of the binary conditioning block is as follows: the number is checked to see if it is less than 0; if so, two's complement is performed and y_neg/A_neg is set high. The same process is applied to the A operand which is also run through its own binary to BCD converter so it can also be shown on the seven segment display.

One last feature of the Math block is its ability to store the computed answer back into the A operand. When the controller sends the Answer_store signal it'll loop the Answer_temp signal back to the operand A register for storage. This allows the user to chain answers into new equations following a calculation.

Please refer to Computation Testbench (Figure 20) in Appendix 3 for an in-depth example of operation.

2.3.7 Binary to BCD

The binary to BCD block is necessary to convert the signed binary number, the calculation form, into sets of Binary Coded Decimal bytes, which are sent to the 7-segment display for output. (See Figure 10 in Appendix 1 for Binary to BCD Converter). This is done according to the Double Dabble algorithm. (https://en.wikipedia.org/wiki/Double_dabble) The binary to BCD converter takes in a 10-bit unsigned value. The output will be three 4-bit numbers that correspond to the three digits of the associated decimal number. (0000 0000 0000, with the first group of four representing the 100s digit and the third group of four representing the 1s digit). The most significant bit of the binary number gets shifted into the least significant bit of the 12 BCD bits. Then the binary number is shifted over so there is a new msb. This occurs 12 times. If at any point a group of 4 has a value greater than or equal to 5, 3 is added to it. This is implemented with multiplexers and a state machine. (Initially loads all the digits in, then shifts and checks if anything is greater than or equal to 5 each time). (See Figure 14 in Appendix 2 for the Binary to BCD State Diagram.) Each time a shift occurs, a shift count is incremented. Once 10 shifts have occurred, the 3 BCD numbers are outputted.

(See Figure 21 in Appendix 3 for the simulation of binary to BCD).

2.3.8 Display

(See Figure 11 in Appendix 1 for Display Block Diagram).

Although we now have all of our desired signals in the form that is transferable to the seven segment display; we'll need some sort of way to select which signal is displayed at any given time. And by focusing on the keyword "select" we immediately understood that we should use a multiplexer to do this job. There are 4 seven segment displays that we have programmed to take a 5-bit input determining their output. Including the decimal point to signify the current operator and we have a total of 5 inputs to shuttle to the seven segments. Furthermore, we have four potential outputs to display at any given time: the digits and operators being inputted by the user, the answer, the answer and the operator the user is inputting (for chaining), and an overload sequence for when the answer is too big.

An RTL design of this block can be seen in the figure above, as you see, the first round of signal selection is conducted by the signal_output signal from the controller. This clarifies what section of the equation the system is currently in and selects the appropriate output.

Two multiplexers follow this selection, each of which are for the additional button features that allow the user to view each operand of the equation. Signals button_A and button_B represent the top and bottom buttons on the FPGA board and when pressed will select the corresponding operand to be displayed on the seven segments. It should also be noted that selection of operand A has priority over operand B as seen in the figure above.

This same sort of selection process is used to determine which LED should light up in the calculator sequence. As you progress through the calculator, the signal LED_output will count from 1 to 4 indicating if the user needs to input operand A, an operator, operand B, or what to do with the answer.

3 Evaluation

3.1 Functionality

The goal of this project was to design and build a functioning calculator using what we've learned from ENGS31. Specifically, we were tasked with creating a calculator that could receive external keyboard inputs, perform the basic mathematical operations, and display our answer on seven segment displays. With those criteria (and some we created) we were very much successful in our endeavour.

Our calculator works almost exactly as we planned it to; it takes in numbers from a keyboard and actively displays them on the seven segments. These numbers then form our operands and can be applied to the main mathematical operations with the answer successfully being displayed.

Within the provided time frame for design we were also able to add additional features to help users and increase functionality. We made it so both positive and negative numbers can be processed. Added LED

sequencing to notify the user their current state within the equation. Allowed the user to check their A and B operands after calculating their answer. Handle potential answer overflow scenarios. And gave the users the option to chain answers into another equation for more options.

3.2 Review

Looking back on the construction of the calculator there were a lot of aspects that were really cool to work on. Figuring out the seven segment displays and being able to control their output using the FPGA buttons was really nice. We originally included this feature as a way to debug our code; such that we could check each intermediate signal to see how our numbers changed as they flowed through the system. Upon completion we adapted it slightly to offer some useful information for our user. It was also interesting (and a little bit challenging) to get the system to work with both positive and negative numbers. Casting the variables into unsigned, doing the computation, and translating/resizing the back proved to be more of a challenge than we expected but it was ultimately very cool to see working.

One functionality that we failed to implement was the ability to receive serial signals from the FPGA and display them back on the computer monitor. We ran into many issues with converting the signals back into ASCII codes and getting the timing working for the components to work together. In the end we were unfortunately unsuccessful with this plan and were forced to redesign the display location to the seven segments on the FPGA. But even with this setback, it was really amazing to design a project from the ground up and get to use everything I've learned thus far into making it work.

4 Conclusions

The initial goal of our project was to create a calculator with computer numeric input and computer numeric output that could handle addition, subtraction, multiplication, and division of positive and negative numbers for results up to 3 digits. Our final product is a calculator that uses computer input to add, subtract, multiply, and divide positive or negative numbers. The output is displayed instead on the 7-segment display of the FPGA. We added usability features such as LED status lights and buttons to review inputs. Therefore, the functionality of our design was exactly the same as in our proposal. We chose to output our results differently because we found that sending data back to the computer was not working well. Using the FPGA outputs allowed our design to look more like a calculator and to have the added LED and button features. Future groups considering this project should work on testing the hardware/computer connection early, as this is actually somewhat difficult. It also allows them to see what the system is outputting, which is helpful for debugging. Additionally, connecting the 7-segment display for debugging purposes is very useful for monitoring what is happening at every step of the calculation process. Overall, implementing ways to assess what is happening within the design is essential. Whereas with computer coding it is possible to have the computer print values, with digital design, it is necessary and important to implement a hardware equivalent.

5 Acknowledgements

In this project Sarah worked on the design and construction of the UART and serial communication of the computer with the calculator. Likewise, she also designed the data conversion between Binary to BCD using the double dabble algorithm. Gavin was tasked with the main controller and datapath of calculator and how it would sort and process inputs from the user. He also designed the Math block and how to chain answers into new equations. Both team members worked together to debug, testbench, and implement every aspect of the program and worked together to design an intuitive display and additive features for the users.

We would also like to thank Ben Dobbins, Professor Eric Hansen, and our TA Yefri for their help and guidance during the constructs of this calculator.

6 References

For the binary to BCD conversion process: https://en.wikipedia.org/wiki/Double_dabble

The Calculator
Group 9 - Gavin Burns and Sarah Hutchinson

System Flow



The diagram illustrates the system architecture and signal flow:

- UART Input:** Receives `serial_input` and outputs `par_output` to the ASCII Converter.
- ASCII Converter:** Outputs control signals (`valid_int`, `valid_op`, `valid_neg`, `enter`, `dit`) to the Main Controller. It also outputs `dig_code` and `op_code` to the Main Datapath.
- Main Datapath:** Receives `dig_en`, `dig_clr`, `neg_en`, `op_en`, `op_clr`, and `op_full` from the Main Controller. It outputs `op`, `neg`, `num2`, `num1`, and `num0` to the Math Block.
- Main Controller:** Manages the flow of data and control signals. It outputs `A_en`, `B_en`, `math_en`, `answer_store`, `answer_full`, and `overflow` to the Math Block. It also outputs `signal_output` and `LED output`.
- Math Block:** Performs mathematical operations. It outputs `A_output`, `A_neg`, `answer`, and `y_neg` to the Binary to BCD (A Operand) converter. It also outputs `answer_full` and `overflow` to the Main Controller.
- Binary to BCD (A Operand):** Converts the operand to BCD, outputting `A2`, `A1`, and `A0`.
- Binary to BCD (Answer):** Converts the answer to BCD, outputting `y2`, `y1`, and `y0`.

9

Math Block Diagram

 


Figure 9: RTL design of the Math function block. num0, num1, num2, and neg are signals from the Datapath that are converted into a signed binary number and stored in either operand A or B. At the command of the Controller, the math block will compute an answer using the inputted operands and operator; and before outputting the signal, will separate the answer into an unsigned binary number and its negativity. Additionally, operand A can be converted in the same fashion for display on the seven segments and the answer can be stored back into operand A for chaining equations.

 


Figure 10: Block diagram for Binary to BCD Conversion. 10-bit binary converted to BCD via the Double Dabble Algorithm, which involves shifting the 10-bit binary input into 3 sets of 4 bit numbers (BCD) and adding 3 if the value of a 4 bit group is ever greater than or equal to 5.

Display Block Diagram

 


Figure 11: Diagram for the seven segment display output. During the typical process of the calculator, the controller will send signals to the first multiplex to determine what data to display. The user also has the option to press the top and bottom button on the FPGA to display the current A and B operands respectively.

Appendix 2. State Diagrams

UART State Diagram

 


Figure 12: UART State Diagram

Calculator State Diagram

 


Figure 13: State diagram of the main controller. The flow of the controller is split up into 4 main sections with conditioning states in between. Each of the sections in state machine represent holding areas that are waiting on user input to process data and move to the next sections. The blue represents inputting operands, the yellow is inputting operators, the green is from answer computation, and the red is designated for chaining equations together

Binary to BCD State Diagram

 


Figure 14: Binary to BCD State Diagram

Appendix 3: Testbench Waveforms

UART Testbench

 


Figure 15: Simulation waveform of our UART converter. Serial signal is delivered in reverse to the UART converter. 1)When the serial input goes low the block is trigger to begin shifting in numbers. 2)In between shifts the values are held constant for the duration of the baud rate. Counter is active for this period and the system is held in the Count.Baud state. 3)Signal is being fed in reverse order into the UART. 4) When the maximum number of shifts is reached, the shifted values are sent out as a parallel signal. The parallel out signal is taken from the shift_signal[8 downto 1].

ASCII Converter Testbench 1

 


Figure 16: Simulation waveform of the ASCII converter. 1)entr signal goes high when enter key is pressed. 2)dlt(spacebar) signal goes high when delete key is pressed

ASCII Converter Testbench 2

 


Figure 17: Simulation waveform for the ASCII converter. 1)Asterisks key ASCII code is recognized; valid_op goes high and op code gains the signal for multiplication. 2)Plus key ASCII code; addition stored. 3)Subtraction key ASCII code; subtraction stored and valid_neg goes high. 4)Slash key ASCII code; division is stored. 5)As digits are recognized, their binary form is stored in dig_code and valid_int goes high

Calculator Controller Testbench

 


Figure 18: Simulation waveform for the main calculator controller. 1)The "operand A" state; where the user can input any 3 digit integer. 1a)When valid_dlt and valid_int signals are detected controller will output dig_dlt and dig_en to add/remove stored digits. A max of 3 digits can ever be stored. 1b)Detection of a valid_op signal has no effect in this state. 1c)Progression to the next state is enacted with the entr signal. 2)The "operator" state. 2a)detecting a valid_int and valid_neg signals have no effect in this state. 2b)Detecting a valid_op will enable op storage and signal that an operator is full. 3)The "operand B" state, same as "operand A" state. 4)Answer state, inputs of previous states our processed and an answer is calculated. 4a)When state is entered math.en goes high and an answer is generated. 4b)Upon leaving state, all currently stored variables are cleared. 5)As the system progresses through different states, it signals to the seven segment display what should be shown.

Calculator Datapath Testbench

 


Figure 19: Simulation waveform of the main calculator datapath. 1)When a dig_en signal is detected, current dig_code is stored in the num0 register and currently stored dig_codes are shifted over in place. 2)dig_dlt signals will delete the dig_code stored in num0 and shift other codes back. 3)neg_en will toggle the negativity of a number. 4)dig_clr will wipe all number and negativity registers. 5)op_en and op_clr store and delete operators respectively. op_full is only high if an operator is present and op_clr has not been pressed

Computation Testbench

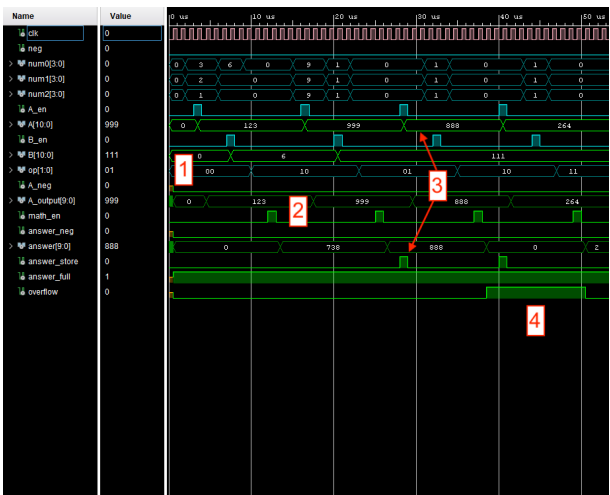


Figure 20: Simulation waveform of computation block; where previous inputs are processed and an answer is output. 1)A.en and B.en take the current BCD numbers, compute them into binary and store them in the A and B operands respectively. 2)When math.en triggers, the system will take the current values of A and B, along with the current operator and calculate and answer. 3)When answer.store is detected, previous answer is stored in the A operand and can be used for recursion. 4)When an answer exceeds the bounds (-999 to 999) the answer will be set to zero and the overflow signal will go high.

Binary to BCD Testbench



Figure 21: Simulation waveform of the BCD to binary converter. 1)When answer_full goes high converter begins shifting in binary_signal. 2)Between each shift the current BCD variables are checked to see if they are greater than 5. If so, the converter adds 3 to them an continues with the shifts. 3)Upon all shifts being conducted each BCD bin is filled with their respective quantity. In this waveform, the number coming in was 999 and the output was a 9, 9, and 9.

Appendix 4: VHDL Programs

UART Input Code

```
1 -----
2 -- Company: Thayer School of Engineering
3 -- Engineer: Gavin Burns & Sarah Hutchinson
4 --
5 -- Create Date: 08/14/2021 12:37:03 AM
6 -- Design Name:
7 -- Module Name: ASCII_converter - behavior
8 -- Project Name: ENGS31 - [REDACTED]
9 -- Target Devices: Basys3 FPGA
10 -- Tool Versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20
21 library IEEE;
22 use IEEE.std_logic_1164.all;
23 use ieee.numeric_std.all;
24
25 entity UART_input is
26 port(
27   clk_port:      in std_logic; -- 1 MHz serial clock
```

```

28 serial_input: in std_logic; --inupt from the keyboard
29 par_output:   out std_logic_vector(7 downto 0); --output signal
30
31 par_output_check: out std_logic_vector(7 downto 0)); --for debugging
32
33 end UART_input
34 architecture behavior of UART_input is
35     constant MAXTIME:      integer := 8; -- ~1 MHz /115,200 baud
36     constant MAXSHIFT:     integer := 10; --shift 10 times
37     signal time_count:      unsigned(13 downto 0) := (others => '0'); --keeps track of time
38     signal shift_count:     unsigned(4 downto 0) := (others => '0'); --keeps track of number
    of shifts
39     signal shift_values:    std_logic_vector(9 downto 0) := (others => '0'); --currently
    shifting values
40
41     signal hold:            std_logic := '0'; --passes the shifting process
42     signal shift_en:        std_logic := '0'; --enables shift_values to be shifted
43     signal load_en:         std_logic := '0'; --loads current values into par_out_temp
44     signal clr:             std_logic := '0'; --clears all currently held values
45
46     signal count:           std_logic := '0'; --keeps track of time between shifts
47     signal timeout:         std_logic := '0'; --signals when MAXTIME has been reached
48     signal count_reset:     std_logic := '0'; --resets the count
49
50     signal Dsync:           std_logic := '1'; --Synchronizes incoming signal
51     signal Dout:            std_logic := '1'; --
52     signal Start:           std_logic := '1'; --signals the start of the reading
53
54     signal first_bit:        std_logic := '0';
55     signal par_out_temp:     std_logic_vector(7 downto 0); --temporarily holds the parallel out
    signal
56
57     type state_type is (idle, count_baud_1, shift_bits_1, count_baud, shift_bits, load, done
    ); --7 state machine
58     signal curr_state:       state_type := idle; --begin in Idle
59     signal next_state:       state_type;
60
61
62 begin
63
64     synchronizer: process(clk_port) --synchronizes the incoming signal
65     begin
66         if rising_edge(clk_port) then
67             Dsync <= serial_input;
68             Dout <= Dsync;
69         end if;
70     end process synchronizer;
71
72     FSM_inc: process(clk_port) --moves through the state machine at the rising edge of the
    clock
73     begin
74         if rising_edge(clk_port) then
75             curr_state <= next_state;
76         end if;
77     end process FSM_inc;
78
79
80     FSM_comb: process(curr_state, timeout, Start, shift_count)
81     begin
82         next_state <= curr_state; --default values
83         shift_en <= '0';
84         load_en <= '0';
85         hold <= '0';
86         count <= '0';
87         count_reset <= '0';
88         first_bit <= '0';
89         clr <= '0';
90
91         case curr_state is
92             when idle =>
93                 count_reset <= '1'; --reset count
94
95                 if Start = '0' then --if incoming signal goes low
96                     next_state <= count_baud_1; --move to Count_Baud_1(start shifting in
    bits)
97                 end if;
98
99                 when count_baud_1 =>
100                     count <= '1'; --begin counting(for baud rate)
101                     first_bit <= '1';
102                     hold <= '1'; --hold onto current value
103
104                     if timeout = '1' then --when MAXCOUNT is reached
105                         next_state <= shift_bits_1; --move to Shift_Bits_1
106                     end if;
107
108                     when shift_bits_1 =>
109                         shift_en <= '1'; --shift in new bit
110                         first_bit <= '1';
111
112                         next_state <= count_baud; --else move to count Baud

```

```

113
114     when count_baud =>
115         count <= '1'; --begin counting(for baud rate)
116         hold <= '1'; --hold current values
117
118         if timeout = '1' then --when MAXCOUNT is reached
119             next_state <= shift_bits; --move to Shift_Bits
120         end if;
121
122     when shift_bits =>
123         shift_en <= '1'; --shift in new bit
124
125         if shift_count >= (MAXSHIFT-1) then --if shift_count is greater than
126             next_state <= load; --move to Load state
127         else
128             next_state <= count_baud; --else move to count Baud
129         end if;
130
131     when load =>
132         load_en <= '1'; --load in currently shifted values
133
134         next_state <= done; --move to Done
135
136     when done =>
137         clr <= '1'; --clear all currently held values(get ready for next set of values
138     )
139
140         next_state <= idle; --move to Idle
141
142     end case;
143 end process FSM_comb;
144
145 shift_counter: process(clk_port, shift_en, hold) --counts the number of shifts
146 begin
147     if rising_edge(clk_port) then --on rising edge
148         if hold = '1' then --if hold is high
149             shift_count <= shift_count; --hold values
150         elsif shift_en = '1' then --if shift_en is high
151             shift_count <= shift_count + 1; --increment shift count
152         else
153             shift_count <= (others => '0'); --else, reset count
154         end if;
155     end if;
156 end process;
157
158 timer: process(clk_port, count_reset, first_bit, time_count, count) --counts for baud rate
159 begin
160     if rising_edge(clk_port) then --on rising edge
161         if count = '1' then --if count is high
162             time_count <= time_count + 1; --increment time_count
163         if first_bit = '1' then --if this is the first bit
164             if time_count >= (MAXTIME/2 - 3) then --set timeout a little sooner
165                 timeout <= '1';
166                 time_count <= (others => '0'); --reset count
167             else
168                 timeout <= '0';
169             end if;
170         else --if not the first bit
171             if time_count = (MAXTIME - 2) then --timeout triggers at normal rate
172                 timeout <= '1';
173                 time_count <= (others => '0');
174             else
175                 timeout <= '0';
176             end if;
177         end if;
178         time_count <= time_count; --default
179     end if;
180
181     if count_reset = '1' then --if count_reset is high
182         time_count <= (others => '0'); --reset time_count
183     end if;
184 end if;
185 end process timer;
186
187 RTL: process(clk_port) --controls the shifting and loading of the bits
188 begin
189     if rising_edge(clk_port) then --on rising edge
190         if Dout = '0' then --if Dout goes low
191             Start <= '0'; --Start mimics
192         else
193             Start <= '1'; --else, Start also mimics
194         end if;
195
196         if shift_en = '1' then --if shift_en is high
197             shift_values <= Dout & shift_values(9 downto 1); --take in new value and right
198         shift
199         else
200             shift_values <= shift_values; --else, hold current value
201         end if;

```

```

201
202         if(clr = '1') then --if clear is high (priority)
203             par_out_temp <= (others => '0'); --clear currently stored values
204         elsif load_en = '1' then --if load is high
205             par_out_temp <= shift_values(8 downto 1); --load bits into par_out_temp
206             par_output_check <= shift_values(8 downto 1); --just for debugging(lets us see
the values being input)
207         else
208             par_out_temp <= par_out_temp; --else, hold current values
209         end if;
210
211         par_output <= par_out_temp; --at the end of the cycle output the newly loaded
values
212     end if;
213 end process RTL;
214
215 end behavior;

```

ASCII_Converter Code

```
1 -----
2 -- Company: Thayer School of Engineering
3 -- Engineer: Gavin Burns & Sarah Hutchinson
4 --
5 -- Create Date: 08/16/2021 09:33:50 AM
6 -- Design Name:
7 -- Module Name: ASCII_converter - behavior
8 -- Project Name: ENGS31 - [REDACTED]
9 -- Target Devices: Basys3 FPGA
10 -- Tool Versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20
21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24 use IEEE.NUMERIC_STD.ALL;
25
26 -- Uncomment the following library declaration if instantiating
27 -- any Xilinx leaf cells in this code.
28 --library UNISIM;
29 --use UNISIM.VComponents.all;
30
31 entity ASCII_converter is
32     Port ( clk: in STD_LOGIC; -- 1 MHz
33           ASCII_code : in STD_LOGIC_VECTOR(7 downto 0); --8bit ASCII code from serial
34
35           op_code : out STD_LOGIC_VECTOR(1 downto 0); --operator code for (+ - * /)
36           dig_code : out STD_LOGIC_VECTOR(3 downto 0); --digit code for (0-9)
37           valid_int : out STD_LOGIC;--signal valid integer
38           valid_op : out STD_LOGIC; --signals valid operator
39           valid_neg : out STD_LOGIC; --signals negative symbol
40           entr : out STD_LOGIC; --signals enter key
41           dlt : out STD_LOGIC); --signals delete key
42 end ASCII_converter;
43
44 architecture behavior of ASCII_converter is
45
46 begin
47
48     ASCII_converter: process(clk)
49     begin
50
51         if rising_edge(clk) then
52             case ASCII_code is
53
54                 when "00100000" => --delete key
55                     dlt <= '1'; --delete code
56
57                 when "00001000" => --backspace key
58                     dlt <= '1'; --delete code
59
60                 when "00001010" => --enter key
61                     entr <= '1'; --enter code
62
63                 when "00101011" => --plus key
64
65                     valid_op <= '1';
66                     op_code <= "00"; --addition code
67
68                 when "00101101" => --minus key
69                     valid_neg <= '1';
70                     valid_op <= '1';
71                     op_code <= "01"; --subtraction code
72
73                 when "00101010" => --asterisks key
74                     valid_op <= '1';
75                     op_code <= "10"; --multiplication code
76
77                 when "00101111" => --slash key
78                     valid_op <= '1';
79                     op_code <= "11"; --division code
80
81                 when "00110000" => --0 key
82                     valid_int <= '1';
83                     dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
84
85                 when "00110001" => --1 key
86                     valid_int <= '1';
87                     dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
88
89                 when "00110010" => --2 key
```

```

90         valid_int <= '1';
91         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
92
93     when "00110011" => --3 key
94         valid_int <= '1';
95         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
96
97     when "00110100" => --4 key
98         valid_int <= '1';
99         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
100
101     when "00110101" => --5 key
102         valid_int <= '1';
103         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
104
105     when "00110110" => --6 key
106         valid_int <= '1';
107         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
108
109     when "00110111" => --7 key
110         valid_int <= '1';
111         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
112
113     when "00111000" => --8 key
114         valid_int <= '1';
115         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
116
117     when "00111001" => --9 key
118         valid_int <= '1';
119         dig_code <= ASCII_code(3 downto 0); --take the last 4 digits
120
121     when others =>
122         --op_code <= (others => '0');
123         --dig_code <= (others => '0');
124         valid_int <= '0'; --set them all off for all other cases
125         valid_op <= '0';
126         valid_neg <= '0';
127         entr <= '0';
128         dlt <= '0';
129     end case;
130 end if;
131 end process;
132 end behavior;

```

Num_Controller Code

```
1 -----
2 -- Company: Thayer School of Engineering
3 -- Engineer: Gavin Burns & Sarah Hutchinson
4 --
5 -- Create Date: 08/11/2021 11:39:17 AM
6 -- Design Name:
7 -- Module Name: num_controller - behavior
8 -- Project Name: ENGS31 - [REDACTED]
9 -- Target Devices: Basys3 FPGA
10 -- Tool Versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20
21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24 use IEEE.NUMERIC_STD.ALL;
25
26 -- Uncomment the following library declaration if instantiating
27 -- any Xilinx leaf cells in this code.
28 --library UNISIM;
29 --use UNISIM.VComponents.all;
30
31 entity num_controller is
32     generic(
33         NUM_DIGITS: integer:= 3); --control the largest number of digits
34     Port ( clk: in STD_LOGIC; --clock signal
35           valid_int : in STD_LOGIC; --signals valid integer
36           valid_op : in STD_LOGIC; --signals valid operator
37           valid_neg : in STD_LOGIC; --signals valid negative symbol
38           entr : in STD_LOGIC; --signals enter key
39           dlt : in STD_LOGIC; --signals delete key
40           op_full : in STD_LOGIC; --signals that an operator has been input
41           answer_full : in STD_LOGIC; --signals that an answer has been computed
42           overflow : in STD_LOGIC; -- signals that the answer has overflown
43
44           dig_en : out STD_LOGIC; --enables digit storage
45           dig_dlt : out STD_LOGIC; --deletes least significant digit
46           dig_clr : out STD_LOGIC; --clears all digit registers
47           op_en : out STD_LOGIC; --enables operator storage
48           op_clr : out STD_LOGIC; --clears operator register
49           neg_en : out STD_LOGIC; --toggles number negativity
50           A_en : out STD_LOGIC; --enable storage into the A operand
51           B_en : out STD_LOGIC; --enables storage into the B operand
52           math_en : out STD_LOGIC; --enables computation
53           LED_output: out STD_LOGIC_VECTOR(1 downto 0); --determines what is output to the
           computer
54           signal_output: out STD_LOGIC_VECTOR(1 downto 0); --determines what is output to
           the computer
55           answer_store: out STD_LOGIC); --stores the operand in operand A
56
57 end entity;
58
59 architecture behavior of num_controller is
60
61     type state_type is (Empty, StoreDigit, StoreNeg, DeleteDigit, LoadA, LoadB, WaitOperator
62     , StoreOperator, DeleteOperator, Clear, Restart, Compute, oops, Idle, AnswerBuffer,
63     AnswerWaitOperator, AnswerStoreOperator, AnswerDeleteOperator); --13 states
64     signal curr_state: state_type:= Empty; -- start in EMPTY state
65     signal next_state: state_type;
66
67     signal count: unsigned(2 downto 0):= (others => '0'); --counts the number of times a
68     digit has been entered (MAX 3)
69     signal output_temp: std_logic_vector(1 downto 0):= (others => '0');
70     signal count_en: std_logic:= '0'; --enables count increment
71     signal count_reset: std_logic:= '0'; --signal to reset counter
72     signal dir: std_logic:= '0'; --determine if count goes up or down
73     signal TC: std_logic:= '0'; --output signal when max is reached
74
75     signal FLAG_en: std_logic:= '0'; --enable FLAG toggle
76     signal FLAG: std_logic:= '0'; --determines which operand
77
78 begin
79     Controller_Update: process(clk)
80     begin
81         if rising_edge(clk) then
82             curr_state <= next_state; --move to next state at the start of the next clock
83             cycle
84         end if;
85     end process;
86
87 end;
```

```

84 Controller_Logic: process(curr_state, valid_int, valid_op, valid_neg, entr, dlt, op_full
, answer_full, TC, FLAG, overflow, output_temp)
85 begin
86     next_state <= curr_state; --default values
87     dig_en <= '0';
88     dig_dlt <= '0';
89     dig_clr <= '0';
90     op_en <= '0';
91     op_clr <= '0';
92     neg_en <= '0';
93     A_en <= '0';
94     B_en <= '0';
95     math_en <= '0';
96     answer_store <= '0';
97     count_en <= '0';
98     count_reset <= '0';
99     FLAG_en <= '0';
100     dir <= '0';
101     signal_output <= "00";
102     LED_output <= "00";
103
104     case curr_state is
105         when Empty => --begin in empty
106             signal_output <= "00";
107
108             if(FLAG = '1') then
109                 LED_output <= "10";
110             else
111                 LED_output <= "00";
112             end if;
113
114             if ((valid_int AND NOT(TC)) = '1') then --if a number is recognized and the
115 registers aren't filled
116                 next_state <= StoreDigit; --go to STORE_DIGIT
117             end if;
118
119             if (valid_neg = '1') then --if a negative symbol is recognized
120                 next_state <= StoreNeg; --go to STORE_NEG
121             end if;
122
123             if (dlt = '1') then --if delete key is recognized
124                 next_state <= DeleteDigit; --go to DELETE_DIGIT
125             end if;
126
127             if (entr = '1') then --if enter key is recognized
128                 if (FLAG = '1') then --and the flag is raised
129                     next_state <= LoadB; --go to LOAD_B
130                 else --if flag is down
131                     next_state <= LoadA; --go to LOAD_A
132                 end if;
133             end if;
134
135
136         when StoreDigit => --STORE_DIGIT state
137             dig_en <= '1'; --enable digit storage
138
139             count_en <= '1'; --enable counter
140             dir <= '1'; --have it increment +1
141
142             next_state <= Empty; --return to EMPTY
143
144
145         when DeleteDigit => --DELETE_DIGIT state
146             dig_en <= '1'; --enble digit storage
147             dig_dlt <= '1'; --delete lsd and have the numbers shift back
148
149             count_en <= '1'; --enable counter
150             dir <= '0'; --have it increment -1
151
152             next_state <= Empty; --return to EMPTY
153
154
155         when StoreNeg => --STORE_NEG state
156             neg_en <= '1'; --toggle negative sign
157
158             next_state <= Empty; --return to EMPTY
159
160
161         when LoadA => --LOAD_A state
162             A_en <= '1'; --load all current digits into operand A
163             FLAG_en <= '1'; --raise flag; indicates that next operand being stored is B
164
165             next_state <= WaitOperator; --move to WAIT_OPERATOR
166
167
168         when LoadB => --LOAD_B state
169             B_en <= '1'; --load all current digits into operand A
170             next_state <= Compute; --move to COMPUTE; carries out the math operations
171
172

```

```

173     when WaitOperator => --WAIT_OPERATOR state
174         signal_output <= "00";
175         LED_output <= "01";
176
177         if (valid_op = '1') then --if an operator is recognized
178             next_state <= StoreOperator; --go to STORE_OPERATOR
179         end if;
180
181         if (dlt = '1') then --if delete key is recognized
182             next_state <= DeleteOperator; --go to DELETE_OPERATOR
183         end if;
184
185         if ((entr AND op_full) = '1') then --if enter key is recognized and there is
an operator present
186             next_state <= Clear; --move to CLEAR; clears previous digits and gets
ready to store operand B
187         end if;
188
189     when StoreOperator => --STORE_OPERATOR state
190         op_en <= '1'; --store the inputed operator
191
192         next_state <= WaitOperator; --retrn to WAIT_OPERATOR; gives user option to
change operator later
193
194
195     when DeleteOperator => --DELETE_OPERATOR state
196         op_clr <= '1'; --clear currently stored operator
197
198         next_state <= WaitOperator; --return to WAIT_OPERATOR
199
200
201     when Clear => --CLEAR state
202         dig_clr <= '1'; --clear all current g=digits and reset negativity
203
204         count_reset <= '1'; --reset count
205
206         next_state <= Empty; --move to EMPTY
207
208
209     when Compute => --COMPUTE state
210         math_en <= '1'; --compute the ansewer
211
212         if (answer_full = '1') then --when an answer is ready
213             if(overflow = '1') then
214                 next_state <= oops;
215             else
216                 next_state <= Idle;
217             end if;
218         end if;
219
220     when oops =>
221         signal_output <= "11";
222         LED_output <= "11";
223
224         if ((entr OR dlt) = '1') then --if enter or delete is recognized
225             next_state <= Restart; --restart the entire process; begining with
operand A
226         end if;
227
228     when Idle =>
229         signal_output <= "01";
230         LED_output <= "11";
231
232         if (valid_op = '1') then --if operator recognized
233             next_state <= AnswerBuffer; --move to STORE_OPERATOR; skips A operand
since the answer is stored in there
234         end if;
235
236         if ((entr OR dlt) = '1') then --if enter or delete is recognized
237             next_state <= Restart; --restart the entire process; begining with
operand A
238         end if;
239
240     when AnswerBuffer =>
241         answer_store <= '1'; --enable storage of the answer
242         A_en <= '1'; --store the answer in operand A; this lets the user connect
equations together
243         op_clr <= '1'; --clear currently stored operator
244
245         next_state <= AnswerStoreOperator;
246
247     when AnswerWaitOperator => --WAIT_OPERATOR state
248         signal_output <= "10";
249         LED_output <= "01";
250
251         if (valid_op = '1') then --if an operator is recognized
252             next_state <= AnswerStoreOperator; --go to STORE_OPERATOR
253         end if;
254
255         if (dlt = '1') then --if delete key is recognized
256

```

```

257         next_state <= AnswerDeleteOperator; --go to DELETE_OPERATOR
258     end if;
259
260     if ((entr AND op_full) = '1') then --if enter key is recognized and there is
an operator present
261         next_state <= Clear; --move to CLEAR; clears previous digits and gets
ready to store operand B
262     end if;
263
264
265     when AnswerStoreOperator => --STORE_OPERATOR state
266         op_en <= '1'; --store the inputed operator
267
268         next_state <= AnswerWaitOperator; --retrn to WAIT_OPERATOR; gives user
option to change operator later
269
270
271     when AnswerDeleteOperator => --DELETE_OPERATOR state
272         op_clr <= '1'; --clear currently stored operator
273
274         next_state <= AnswerWaitOperator; --return to WAIT_OPERATOR
275
276     when Restart => --RESTART state
277         dig_clr <= '1'; --clear currently stored digits
278         op_clr <= '1'; --clear operator
279         FLAG_en <= '1'; --lower flag; returning to A operand storage
280
281         count_reset <= '1'; --reset count
282
283         next_state <= Empty; --move to EMPTY
284     end case;
285 end process;
286
287 Counter: process(clk, count) --controls the user from pushing out the msd
begin
288     if rising_edge(clk) then
289         if(count_reset = '1') then --if reset count is enabled; priority over count
enable
290
291             count <= (others => '0'); --reset count
292             elsif(count_en = '1') then --else if count is enabled
293                 if(dir = '0' AND NOT(count = 0)) then --and direction is low and count isnt
already at 0
294                     count <= count - 1; --increment -1
295                     elsif (dir = '1' AND count <= NUM_DIGITS) then -- or if direction is high
and count isnt already larger than NUM_DIGITS
296                         count <= count + 1; --increment +1
297                     end if;
298                 end if;
299             end if;
300
301             TC <= '0'; --default value
302             if(count >= NUM_DIGITS) then --if count is higher or equal to than the number of
permitted digits (3)
303                 TC <= '1'; --TC goes high
304             end if;
305         end process;
306
307 FlagPole: process(clk) --toggles the current state of the FLAG indicator
begin
308     if rising_edge(clk) then
309         if (FLAG_en = '1') then
310             FLAG <= NOT(FLAG); --toggle FLAG
311         end if;
312     end if;
313 end process;
314 end behavior;

```

Num_Datapath Code

```
1 -----
2 -- Company: Thayer School of Engineering
3 -- Engineer: Gavin Burns & Sarah Hutchinson
4 --
5 -- Create Date: 08/11/2021 08:13:33 PM
6 -- Design Name:
7 -- Module Name: ASCII_converter_tb - testbench
8 -- Project Name: ENGS31 - [REDACTED]
9 -- Target Devices: Basys3 FPGA
10 -- Tool Versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20
21 library IEEE;
22 use IEEE.std_logic_1164.all;
23
24 entity num_datapath is
25     --generic(
26         --NUM_DIGITS: integer); --control the largest number of digits
27     port(
28         clk: in std_logic; --clock signal
29         dig_code: in std_logic_vector(3 downto 0); --BCD number between 0-9
30         op_code: in std_logic_vector(1 downto 0); --operator code: 00=addition, 01=sub, 10=
31         mult, 11=div
32         dig_en: in std_logic; --enables digit storage
33         dig_dlt: in std_logic; --deletes least significant digit
34         dig_clr: in std_logic; --clears all digit registers
35         op_en: in std_logic; --enable operator storage
36         op_clr: in std_logic; --clears operator register
37         neg_en: in std_logic; --toggles number negativity
38
39         op: out std_logic_vector(1 downto 0); --entered operator
40         num0: out std_logic_vector(3 downto 0); --one's place
41         num1: out std_logic_vector(3 downto 0); --ten's place
42         num2: out std_logic_vector(3 downto 0); --hundred's place
43         neg: out std_logic; --current negativity
44         op_full: out std_logic); --whether an operator is present
45 end num_datapath;
46
47 architecture behavior of num_datapath is
48
49     signal temp_neg: std_logic:= '0'; --for T Flip-Flop
50     signal dig0, dig1, dig2: std_logic_vector(3 downto 0):= (others => '0'); --tmeporary
51     -- signal num0_temp, num1_temp, num2_temp: std_logic_vector(3 downto 0):= (others => '0')
52     ;
53 begin
54     operator: process(clk)
55     begin
56         if rising_edge(clk) then --on the rising edge
57             if(op_en = '1') then
58                 op <= op_code; --store operator
59                 op_full <= '1'; --set operator to full (lets you move to next state
60             end if;
61
62             if(op_clr = '1') then
63                 --op <= others => '0'; --clear operator (default to addition)
64                 op_full <= '0'; --set operator to empty (cannot move on until operator is
65             input)
66             end if;
67         end if;
68     end process;
69
70     negative: process(clk, temp_neg)
71     begin
72         if rising_edge(clk) then --on rising edge
73             if(neg_en = '1') then
74                 temp_neg <= NOT(temp_neg); --toggle negativity
75             end if;
76
77             if(dig_clr = '1') then
78                 temp_neg <= '0'; --reset negativity
79             end if;
80         end if;
81
82         neg <= temp_neg; --output current negativity
83     end process;
84
85     number: process (clk, dig0, dig1, dig2)
86     begin
```

```

86     if rising_edge(clk) then -- on rising edge
87         if(dig_en = '1') then
88             dig0 <= dig_code; --shift msd and store entered digit
89             dig1 <= dig0;
90             dig2 <= dig1;
91         end if;
92
93         if(dig_dlt = '1') then
94             dig0 <= dig1; --delete lsd and shift
95             dig1 <= dig2;
96             dig2 <= (others => '0');
97         end if;
98
99         if(dig_clr = '1') then
100             dig0 <= (others => '0'); --clear all digits
101             dig1 <= (others => '0');
102             dig2 <= (others => '0');
103         end if;
104
105
106         --         num0_temp <= num0_temp;
107         --         num1_temp <= num1_temp;
108         --         num2_temp <= num2_temp;
109
110         --if(busy_convert = '0') then
111             num0 <= dig0; --output current digits
112             num1 <= dig1;
113             num2 <= dig2;
114         --end if;
115
116         --         num0 <= num0_temp;
117         --         num1 <= num1_temp;
118         --         num2 <= num2_temp;
119     end if;
120
121 end process;
122
123 end behavior;

```

Math Code

```
1 -----
2 -- Company: Thayer School of Engineering
3 -- Engineer: Gavin Burns & Sarah Hutchinson
4 --
5 -- Create Date: 08/16/2021 11:43:22 AM
6 -- Design Name:
7 -- Module Name: Math - Behavioral
8 -- Project Name: ENGS31 - Operation_[REDACTED]
9 -- Target Devices: Basys3 FPGA
10 -- Tool Versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20
21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24 use IEEE.NUMERIC_STD.ALL;
25
26 -- Uncomment the following library declaration if instantiating
27 -- any Xilinx leaf cells in this code.
28 --library UNISIM;
29 --use UNISIM.VComponents.all;
30
31 entity Math is
32     Port ( clk: in STD_LOGIC; --clock signal
33           num0: in std_logic_vector(3 downto 0); --one's place
34           num1: in std_logic_vector(3 downto 0); --ten's place
35           num2: in std_logic_vector(3 downto 0); --hundred's place
36           neg: in std_logic; --current negativity
37           op: in STD_LOGIC_VECTOR(1 downto 0); --operator
38           A_en : in STD_LOGIC; --enables storage of number into A operand
39           B_en : in STD_LOGIC; --enables storage of number into B operand
40           math_en : in STD_LOGIC; --enables computation of A and B by op
41           answer_store : in STD_LOGIC; --stores the answer in the A operand
42
43           answer : out STD_LOGIC_VECTOR(9 downto 0); --outputted answer
44           A_output : out STD_LOGIC_VECTOR(9 downto 0);
45           A_neg : out STD_LOGIC;
46           overflow: out STD_LOGIC; --signals that the value is beyond -999 or 999
47           y_neg : out STD_LOGIC; --whether answer is negative or not
48           answer_full : out STD_LOGIC); --signals that an answer is ready to be presented
49 end Math;
50
51 architecture behavior of Math is
52
53     signal A: SIGNED(10 downto 0):= (others => '0'); --Operand A; 11 bits to store numbers
54     signal B: SIGNED(10 downto 0):= (others => '0'); --Operand A; 11 bits to store numbers
55     signal answer_temp: SIGNED(20 downto 0):= (others => '0'); --answer; 21 bits to store
56     --signal num0_temp: UNSIGNED(10 downto 0):= (others => '0');
57     --signal num1_temp: UNSIGNED(10 downto 0):= (others => '0');
58     --signal num2_temp: UNSIGNED(10 downto 0):= (others => '0');
59     --signal num3_temp: UNSIGNED(10 downto 0):= (others => '0');
60     constant I: unsigned(6 downto 0):= "1100100"; --needed for BCD conversion
61
62 begin
63
64     Store: process(clk)
65     begin
66         if rising_edge(clk) then
67
68             --num0_temp(3 downto 0) <= unsigned(num0);
69             --num1_temp <= resize(10*unsigned(num1), num1_temp'length);
70             --num2_temp <= resize(I*unsigned(num2), num2_temp'length);
71             --num3_temp <= resize(10*unsigned(num2_temp), num3_temp'length);
72
73             if (A_en = '1') then
74                 if (answer_store = '1') then
75                     A <= answer_temp(10 downto 0); --store the answer into operand A(for
76                     recursion)
77                 else
78                     if(neg = '1') then --if value is negative
79                         A <= NOT(signed(resize(I*unsigned(num2) + 10*unsigned(num1) +
80                         unsigned(num0), A'length))) + 1; --two's compliment of the digits
81                     else
82                         A <= signed(resize(I*unsigned(num2) + 10*unsigned(num1) + unsigned(
83                         num0), A'length)); --store digits in operand A
84                     end if;
85                 end if;
86             elsif (B_en = '1') then
```

```

84         if(neg = '1') then --if value is negative
85             B <= NOT(signed(resize(I*unsigned(num2) + 10*unsigned(num1) +
            unsigned(num0), B'length))) + 1; --two's compliment of the digits
86         else
87             B <= signed(resize(I*unsigned(num2) + 10*unsigned(num1) + unsigned(
            num0), B'length)); --store digits into operand B
88         end if;
89     end if;
90
91     if(A < 0) then
92         A_neg <= '1'; --separate the negative
93         A_output <= std_logic_vector((NOT(A(9 downto 0)) + 1)); --store the
            value in answer
94     else
95         A_neg <= '0';
96         A_output <= std_logic_vector(A(9 downto 0)); --store the value of answer
97     end if;
98 end if;
99 end process;
100
101 Computation: process(clk, answer_temp)
102 begin
103
104     if rising_edge(clk) then
105
106         answer_full <= '0';
107
108         if (math_en = '1') then
109
110             --answer_temp <= answer_temp;
111
112             case op is
113                 when "00" => --addition operator
114                     answer_temp <= resize(A + B, answer_temp'length); --add A and B
115
116                 when "01" => --subtraction operator
117                     answer_temp <= resize(A - B, answer_temp'length); --subtract B from
            A
118
119                 when "10" => --multiplication operator
120                     answer_temp <= resize(A * B, answer_temp'length); --multiply A and B
121
122                 when "11" => --division operator
123                     answer_temp <= resize(A / B, answer_temp'length); --divide A by B
124
125                 when others =>
126                     answer_temp <= (others => '0'); --set to zero so we can easily see
            there's an error
127             end case;
128
129         end if;
130
131         if(answer_temp > 999 OR answer_temp < -999) then --if the answer is out of
            bounds
132             answer <= (others => '0'); --store the value "1000000000" (indicates an
            overvalued answer)
133             overflow <= '1'; --signal overflow(this value cannot be stored in A)
134             answer_full <= '1'; --signal that an answer has been generated
135         else
136             if(answer_temp < 0) then
137                 y_neg <= '1'; --separate the negative
138                 answer <= std_logic_vector((NOT(answer_temp(9 downto 0)) + 1)); --
            store the value in answer
139             else
140                 y_neg <= '0';
141                 answer <= std_logic_vector(answer_temp(9 downto 0)); --store the
            value of answer
142             end if;
143             overflow <= '0';
144             answer_full <= '1'; --signal that an answer has been generated
145         end if;
146
147     end if;
148 end process;
149
150 end behavior;

```

Binary to BCD Code

```
1 -----
2 -- Company: Thayer School of Engineering
3 -- Engineer: Gavin Burns & Sarah Hutchinson
4 --
5 -- Create Date: 08/17/2021 10:14:52 PM
6 -- Design Name:
7 -- Module Name: ASCII_converter - behavior
8 -- Project Name: ENGS31 - [REDACTED]
9 -- Target Devices: Basys3 FPGA
10 -- Tool Versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20
21
22 library IEEE;
23 use IEEE.std_logic_1164.all;
24 use ieee.numeric_std.all;
25
26 entity binary_BCD is
27     port( clk:          in  std_logic; --clock signal
28           answer_full:   in  std_logic; --signals that an answer has been generated
29           binary_in:     in  std_logic_vector(9 downto 0); --binary answer
30
31           y0:            out std_logic_vector(3 downto 0); --BCD number (0-9) lsd
32           y1:            out std_logic_vector(3 downto 0); --BCD number (0-9) mid digit
33           y2:            out std_logic_vector(3 downto 0)); --BCD number (0-9) msd
34
35 end binary_BCD;
36
37 architecture behavior of binary_BCD is
38     constant NSHIFT:      integer := 10; --number of total shifts
39     signal store_bin:      unsigned(9 downto 0) := (others => '0');
40     signal temp_bcd:       unsigned(11 downto 0) := (others => '0');
41     signal shift_count_en: std_logic := '0'; --enables shift_cout to increment
42     signal shift_count_reset: std_logic := '0'; --resets shift count
43     signal shift_count:    unsigned(5 downto 0) := "000000"; --counts the number of
44     shifts
45     signal load_en:        std_logic := '0'; --loads the answer into the store_bin
46     signal clr:            std_logic := '0'; --clears store bin
47     signal shift_en:       std_logic := '0'; --right shifts the store_bin into the
48     BCD generator
49     signal all_shifted:    std_logic := '0'; --signals that all of the bits have
50     been shifted
51     signal check:          std_logic := '0'; --signals to check if each BCD bin is
52     greater than 5
53
54     type state_type is (idle, load_bin, shift, shift_check);
55     signal curr_state:     state_type := idle;
56     signal next_state:     state_type;
57
58 begin
59
60     RTL: process(clk)
61     begin
62         if rising_edge(clk) then
63
64             if(clr = '1') then
65                 store_bin <= (others => '0');
66                 temp_bcd <= (others => '0');
67             elsif load_en = '1' then
68                 store_bin <= unsigned(binary_in); --load the answer into store_bin
69             else
70                 store_bin <= store_bin;
71             end if;
72
73             if shift_en = '1' then
74                 temp_bcd <= temp_bcd(10 downto 0) & store_bin(9); --left shift bits into BCD
75                 generator
76                 store_bin <= store_bin(8 downto 0) & '0'; --left shift store_bin
77             end if;
78
79             if(check = '1') then
80                 if temp_bcd(3 downto 0) >= 5 then --check if the first BCD bin is >5
81                     temp_bcd(3 downto 0) <= temp_bcd(3 downto 0) + 3; --if so; add 3
82                 else
83                     temp_bcd(3 downto 0) <= temp_bcd(3 downto 0); --else; no change
84                 end if;
85
86                 if temp_bcd(7 downto 4) >= 5 then --check if second BCD bin is >5
87                     temp_bcd(7 downto 4) <= temp_bcd(7 downto 4) + 3; --if so; add 3
88                 else
89                     temp_bcd(7 downto 4) <= temp_bcd(7 downto 4); --else; no change
90                 end if;
91             end if;
92
93             curr_state <= next_state;
94         end if;
95     end process RTL;
96 end behavior;
```

```

85         temp_bcd(7 downto 4) <= temp_bcd(7 downto 4); --else; no change
86     end if;
87
88     if temp_bcd(11 downto 8) >= 5 then --check if third BCD binis >5
89         temp_bcd(11 downto 8) <= temp_bcd(11 downto 8) + 3; --if so; add 3
90     else
91         temp_bcd(11 downto 8) <= temp_bcd(11 downto 8); --else; no change
92     end if;
93 end if;
94
95     if all_shifted = '1' then --once all bits have been shifted
96         y0 <= std_logic_vector(temp_bcd(3 downto 0)); --store first BCD bin in num0 (lsd
97     )
98         y1 <= std_logic_vector(temp_bcd(7 downto 4)); --store second BCD bin in num0 (
99         mid digit)
100        y2 <= std_logic_vector(temp_bcd(11 downto 8)); --store third BCD bin in num0 (
101        msd)
102        --else
103        --num0 <= "0000";
104        --num1 <= "0000";
105        --num2 <= "0000";
106    end if;
107 end if;
108
109 end process RTL;
110
111 FSM_comb: process(curr_state, answer_full, all_shifted)
112 begin
113     next_state <= curr_state;
114     shift_en <= '0';
115     load_en <= '0';
116     clr <= '0';
117     check <= '0';
118
119     shift_count_en <= '0';
120     shift_count_reset <= '0';
121
122     case curr_state is
123     when idle =>
124         shift_count_reset <= '1';
125         clr <= '1';
126
127         if answer_full = '1' then
128             next_state <= load_bin;
129         end if;
130
131     when load_bin =>
132         load_en <= '1';
133
134         next_state <= shift;
135
136     when shift =>
137         shift_en <= '1';
138         shift_count_en <= '1';
139
140         if all_shifted = '1' then
141             next_state <= idle;
142         else
143             next_state <= shift_check;
144         end if;
145
146     when shift_check =>
147         check <= '1';
148
149         if all_shifted = '1' then
150             next_state <= idle;
151         else
152             next_state <= shift;
153         end if;
154     end case;
155 end process FSM_comb;
156
157 counter: process(clk, shift_count, shift_count_reset)
158 begin
159     if rising_edge(clk) then
160         if(shift_count_en = '1') then --else if shift_count is enabled
161             shift_count <= shift_count + 1; --increment shift_count by 1;
162         end if;
163     end if;
164
165     if(shift_count_reset = '1') then --if reset shift_count is enabled; priority over
166     count enable
167         shift_count <= (others => '0'); --reset shift_count
168     end if;
169
170     all_shifted <= '0'; --default value
171     if(shift_count >= NSHIFT) then --if shiftcount is greater than number of required
172     shifts

```

```
171         all_shifted <= '1'; --all_shifted goes high
172         --shift_count <= (others => '0');
173     end if;
174 end process;
175
176 FSM_update: process(clk)
177 begin
178     if rising_edge(clk) then
179         curr_state <= next_state;
180     end if;
181 end process FSM_update;
182
183
184 end behavior;
```

Appendix 5: Residual Warnings

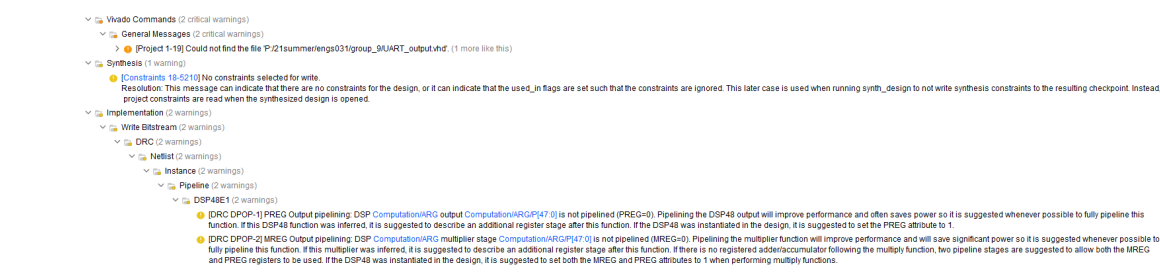


Figure 22: Residual error messages



Figure 23: Zoomed in Residual error messages

We had four residual error messages. The first error message is due to the fact that an earlier version of our project also used a UART_out block to reformat the signals to be outputted back to the computer. However, we ultimately decided to use the 7-segment display for the output instead. Since the UART is no longer part of our project but various testbenches and debugging shells reference the block, an error was produced. There is also a constraints error, however, this is not relevant because we did have constraints selected. Our final two errors are about pipelining. Vivado is suggesting that due to some of the time delays associated with computation, additional registers should be added in the middle of the computation so that the computation delays do not slow down the rest of the system. However, we were not experiencing any errors resulting from this, so we left our design as it was.

Appendix 7: Resource Utilization

 


Figure 24: Resource Utilization

Our design used 2.22% of the look-up tables, 0.69% of the flip-flops, 1.11% of the digital signal processors, and 18.87% of the input/output buffers.