

Week 2 Lab:

1. Make a coplanar waveguide resonator with:
 - a. Characteristic impedance of 50 Ohms.
 - i. **What center conductor width, gap width, dielectric thickness and dielectric constant did you use?**
 - b. Frequency of 7 GHz
 - i. **What length do you need?**
 - c. External quality factor of 1000
2. Given a Josephson inductance of 10 nH, make a qubit with:
 - a. Frequency of 5 GHz.
 - i. **What E_c does this give?**
 - ii. **Is this a transmon?**
3. Make a coupled resonator-qubit system with:
 - a. Coupling strength $g/2\pi = 100$ MHz.
 - i. **How close do the resonator and qubit need to be?**
 - ii. **What dispersive shift would you get?**
4. Make an external drive line with:
 - a. Coupling strength $k/2\pi = 100$ kHz