Lab #2:

- 1. <u>Cables</u>: Measure the transmission across a cable
 - a. Fit the transmission to a line
 - b. Assume the cable loss is linear with frequency. What is the attenuation per unit anlength?
- 2. Filters: Measure the transmission across a low pass filter
 - a. What is the cutoff frequency?
 - b. How does this differ from a basic low pass LC filter?
- 3. <u>Filters</u>: Measure the transmission across a bandpass filter
 - a. What is the high frequency cutoff?
 - b. What is the low frequency cutoff?
 - c. How does this differ from a basic LC bandpass filter?
- 4. Filters: Measure the transmission across high pass filter
 - a. What is the cutoff frequency?
 - b. How does this differ from a basic high pass LC filter?
- 5. <u>Nonreciprocal components</u>: Measure the transmission across a circulator
 - a. Construct the 3x3 scattering matrix
- 6. <u>Nonreciprocal components</u>: Measure the transmission across an isolator
 - a. Construct the 2x2 scattering matrix
 - b. How does the isolator differ from the circulator?
 - c. What happens if you terminate one port with a grounding cap? A 50 ohm cap?